



Compartilhar

0

mais

[Próximo blog»](#)[Criar um blog](#) [Login](#)

1

Monday, January 10, 2011

Memory Module with A Memory Controller

#####Here
is the VHDL code for the Memory Controller
3#####

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Controller is
port( read_write,ready,clock,reset: in std_logic;
      oe,we           : out std_logic);

end Controller;

architecture Behavioral of Controller is
type Statetype is (idle,decision,read1,write1);
signal presentstate, nextstate : Statetype;
begin

    process(presentstate,read_write,ready)
    begin

        case presentstate is
```

```

        when idle => oe<='0'; we<='0';
            if ready='1' then
                nextstate<=decision;
            else
                nextstate<=idle;
            end if;

        when decision => oe<='0'; we<='0';
            if(read_write='1') then
                nextstate<=read1;
            else
                nextstate<=write1;
            end if;

        when read1=> oe<='1'; we<='0';

            if (ready='1') then
                nextstate<=idle;
            else
                nextstate<=read1;
            end if;

        when write1 => oe<='0'; we<='1';
            if (ready='1') then
                nextstate <=idle;
            else
                nextstate<=write1;
            end if;

        end case;

    end process;

    process(reset,clock)
    begin

        if reset='1' then
            presentstate<=idle;

        elsif(clock'event and clock='1') then
            presentstate<=nextstate;
        end if;

    end process;

end Behavioral;

```

```

#####

```

Here is the VHDL code for the top module

```

#####

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ControllingRAM is

port (
    clock : in std_logic;
    datain : in std_logic_vector(11 downto 0);
    dataout : out std_logic_vector(11 downto 0);
    writeaddress : in std_logic_vector(9 downto 0);
    readaddress : in std_logic_vector(9 downto 0);
    read_write : in std_logic;
    ready : in std_logic;
    reset : in std_logic);

end ControllingRAM;

architecture Behavioral of ControllingRAM is

component Controller is

port( read_write,ready,clock,reset: in std_logic;
      oe,we : out std_logic);

end component;

component RAM1KB is

port (clk : in std_logic;
      oe : in std_logic;
      we : in std_logic;
      a : in std_logic_vector(9 downto 0);
      b : in std_logic_vector(9 downto 0);
      di : in std_logic_vector(11 downto 0);
      do : out std_logic_vector(11 downto 0));

end component;

signal oetemp: std_logic;
signal wetemp: std_logic;

begin

u1: RAM1KB port map (

    clk => clock ,
    oe => oetemp,
    we => wetemp,
    a => writeaddress,
    b => readaddress,
    di => datain,
    do => dataout



);

u2: Controller port map
(

    read_write => read_write,
    ready => ready,
    clock => clock,
    reset => reset,
```

```
oe =>    oetemp,  
we =>    wetemp  
  
);  
  
end Behavioral;
```

#####

  

Posted by amr nasr at 1:30 AM
Email ThisBlogThis!Share to TwitterShare to FacebookShare to Pinterest
Labels: Memory Controller, RAM

Newer Post Older Post Home

Your IP and Google Map location

[AdF.ly - shorten money!](#)



Freelancer Sites

Embedded Software Blog

HDfpga

Mobile Dev & Design

vhdlguru

electronics-tech.com

Virtex-5 Resource

Xilinx, Inc.

fpga4fun

Verilog / VHDL Projects

OpenCores

Linux Wiki



VHDL Active Bloggers

Dangerous Prototypes

FPGA Developer
The Digital Electronics Blog
Reconfigurable Computing
Final Year Projects by "www.IndianEngineer.in"
vhdlguru
IndianEngineer
Chip Design Magazine
vsibank
OutputLogic.com
Digital Puzzles and Challenges
FPGA and DSP from scratch
FPGA from Scratch
第4836页 程序源码搜索引擎 - HackChina.com
VLSI FORUM
Digital Design Projects
Essential VHDL: VHDL Design Examples
FPGA - -Verilog www.pudn.com 

Followers